

TABLE OF CONTENTS

Unit No.	Title	Page No.
1	Introduction to Wave Shaping Circuits	1-27
	1.1 Introduction to Clipping and Clamping Circuits	
	1.2 Clippers	
	1.3 Dual Clipper	
	1.4 Clamper Circuits	
2	Amplifiers	28-51
	2.1 Introduction to the Amplifier	
	2.2 Classification of amplifiers	
	2.3 Single-Stage BJT Amplifiers	
	2.4 Amplifier Classes	
	2.5 Amplifier Classes and Efficiency	
3	Oscillators	52-94
	3.1 Introduction to Oscillators	
	3.2 Classification Of Oscillators	
	3.3 Stability criterion	
	3.4 RC Oscillator	
	3.5 Wien Bridge Oscillator	
	3.6 Colpitts Oscillator	
	3.7 Hartley Oscillator	
	3.8 Crystal Oscillators	
4	Special Semiconductor Devices	95-154
	4.1 Introduction to special semiconductor devices	
	4.2 Tunnel Diode	
	4.3 PN Junction	
	4.4 Varactor Diode	
	4.5 Silicon-Controlled Rectifier (Scr)	
	4.6 Two Transistor Model of SCR or Thyristor	
	4.7 Rating of SCR or Thyristor	
	4.8 DIAC:	
	4.9 TRIAC:	
	4.10 UJT	

- 5.1 Introduction To Optoelectronic Devices
- 5.2 LDR
- 5.3 Photovoltaic Cell
- 5.4 Light Activated SCR
- 5.5 Photodiode
- 5.6 Phototransistor
- 5.7 Laser Diode
- 5.8 LED
- 5.9 Charge Coupled Device (CCD)