

TABLE OF CONTENTS

UNIT	TITLE	PAGE NO.
1	SEMICONDUCTOR THEORY AND DIODES	01-35
	1.1 Introduction to Semiconductors	
	1.2 Energy Bands and Charge Carriers	
	1.3 PN Junction Theory	
	1.4 Characteristics of PN Junction Diode	
	1.5 Zener Diode – Working and Applications	
	1.6 Diode as a Rectifier (Half-Wave and Full-Wave)	
	1.7 Clipping and Clamping Circuits	
2	BIPOLAR JUNCTION TRANSISTORS (BJT)	36-65
	2.1 Structure and Operation of BJT	
	2.2 BJT Configurations – CE, CB, CC	
	2.3 Input and Output Characteristics of BJT Configurations	
	2.4 DC Load Line and Q-Point	
	2.5 BJT Biasing Techniques	
	2.6 Stability Factor and Bias Stabilization	
3	FIELD EFFECT TRANSISTORS (FET)	66-94
	3.1 JFET – Construction, Operation, and Characteristics	
	3.2 MOSFET (Enhancement and Depletion Mode)	
	3.3 Comparison between JFET and MOSFET	
	3.4 Biasing of FETs	
	3.5 FET as an Amplifier	
	3.6 CMOS Technology Basics	
4	AMPLIFIERS AND FEEDBACK	95-124
	4.1 Small Signal Amplifiers – CE, CC, and CS	
	4.2 Voltage Gain, Current Gain, and Power Gain	
	4.3 Frequency Response of Amplifiers	
	4.4 Multistage Amplifiers	
	4.5 Negative Feedback Amplifiers – Types and Benefits	
	4.6 Feedback Topologies and Their Effects	

5	OSCILLATORS AND POWER AMPLIFIERS	125-152
	5.1 Conditions for Oscillations – Barkhausen Criteria	
	5.2 RC Phase Shift Oscillator	
	5.3 Hartley and Colpitts Oscillators	
	5.4 Crystal Oscillator	
	5.5 Classification of Power Amplifiers (Class A, B, AB, C)	
	5.6 Push-Pull and Complementary Symmetry Amplifiers	
6	SPECIAL SEMICONDUCTOR DEVICES	153-172
	6.1 SCR – Operation and Applications	
	6.2 DIAC and TRIAC – Construction, Operation, and Applications	
	6.3 UJT – Characteristics and Applications	
	6.4 Photodiodes, Phototransistors, and LED – Construction, Operation, and Applications	
	6.5 Opto-Couplers and Their Applications	