

TABLE OF CONTENTS

Chapter No.	Title	Page No.
1	Operational Amplifier Fundamentals	01-24
	1.1 Historical Background	
	1.2 Introduction	
	1.3 Operational Amplifiers	
	1.4 Ideal Op-amp characteristics	
	1.5 Differential Amplifier	
	1.6 Op-amp parameters	
	1.7 Frequency response and stability considerations	
2	Linear Applications of Op-amp	25-50
	2.1 Introduction	
	2.2 Inverting and Non-inverting amplifier	
	2.3 Voltage Follower	
	2.4 Summing Amplifier	
	2.5 Integrator	
	2.6 Differentiator	
	2.7 Instrumentation Amplifier	
	2.8 Voltage-to-Current and Current-to-Voltage Converters	
3	Non-linear Applications of Op-amp	51-87
	3.1 Non-linear applications	
	3.2 Comparator	
	3.3 Zero Crossing Detector Circuit	
	3.4 Schmitt Trigger	
	3.5 Precision Rectifier	
	3.6 Peak Detector	
	3.7 Sample and Hold Circuit	
	3.8 Logarithmic and Anti-logarithmic Amplifier	
	3.9 Clippers and Clampers	
4	Oscillators and Waveform Generators	88-123
	4.1 Introduction	
	4.2 RC Phase -Shift Oscillator	
	4.3 Wien Bridge Oscillator	

- 4.4 Square Wave Generator
- 4.5 Triangular Wave Generator using Op-amp
- 4.6 Saw tooth Generator
- 4.7 Monostable and Astable Multivibrator
- 4.8 555 Timer

5

Analog Multipliers and Phase-Locked Loops

124-137

- 5.1 Introduction
- 5.2 Analog Multipliers
- 5.3 Phase-Locked Loop
- 5.4 Voltage-Controlled Oscillator